

$$\textcircled{5.} \quad C_{eq} = 2100 \cdot 5 \mu F \\ = 10,5 \text{ mF}$$

$$C_{eq} = \frac{Q}{V}$$

$$10,5 \text{ mF} \cdot 55000 = Q$$

$$Q = 577,5 \text{ [C]}$$