

$$\textcircled{6:} \quad \frac{1}{C_{eq}} = \left(\frac{1}{2,12} + \frac{1}{3,80} \right) \frac{1}{10^{-6}}$$

$$C_{eq} = 1,37 \cdot 10^{-6} \text{ F.}$$

$$u = \frac{1}{2} C V^2$$

$$= \frac{1}{2} \cdot 1,37 \mu\text{F} \cdot 328^2$$

$$= 0,0736 \text{ [J]}$$