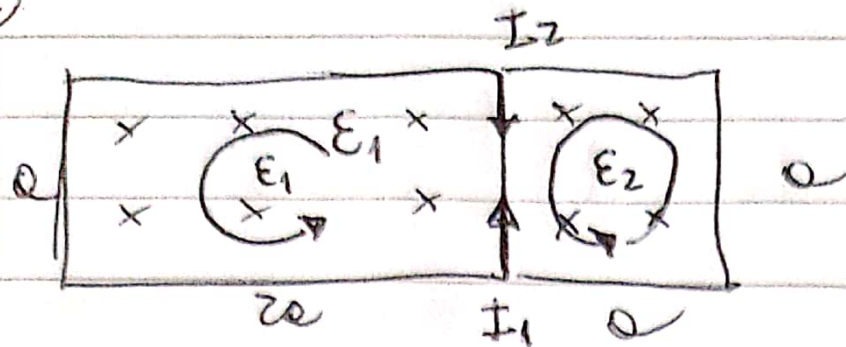


3.



B aumenta en t
 ϕ aumenta con " t "

$$A_1 = 2a^2$$

$$A_2 = a^2$$

$$\phi = \int B dA$$

$$\phi = 0,001t \cdot a^2$$

$$= BA$$

$$= 0,001t \cdot 2a^2$$

$$l_1 = 5a$$


$$l_2 = 3a$$

$$l_3 = a$$

$$\mathcal{E} = -d\phi/dt \Rightarrow A_1 \Rightarrow \mathcal{E}_1 = -2 \cdot 0,001 \cdot a^2$$

$$R_i = 0,1 \cdot l_i = -0,845 \text{ [mV]}$$
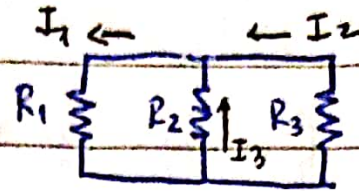
$$A_2 \Rightarrow \mathcal{E}_2 = -0,423 \text{ [mV]}$$



$$R_1 = 0,1 \cdot (5 \cdot 0,65)$$

$$R_2 = 0,1 \cdot (3 \cdot 0,65)$$

$$R_3 = 0,1 \cdot (0,65)$$

$$R_1 = 0,1 \cdot \frac{\Omega}{m} \cdot 5 \cdot 0,65 \text{ m} = 0,325 \Omega$$

$$R_2 = 0,1 \cdot 3 \cdot 0,65 = 0,195 \Omega$$

$$R_3 = 0,1 \cdot 0,65 = 0,065 \Omega$$

$$|\mathcal{E}_1| - I_1 R_1 - I_3 R_2 = 0 \quad ; \quad 0,845 \cdot 10^{-3} - 0,325 I_1 - 0,195 I_3 = 0$$

$$|\mathcal{E}_2| + I_3 R_2 - I_2 R_3 = 0 \quad ; \quad 0,423 \cdot 10^{-3} + 0,195 I_3 - 0,065 I_2 = 0$$

$$I_3 + I_2 = I_1$$

$$I_3 + I_2 = I_1$$

$$I_1 = 3,11 \text{ [mA]}$$

$$I_2 = 3,96 \text{ [mA]}$$

$$I_3 = -0,85 \text{ [mA]}$$

↓ I₃