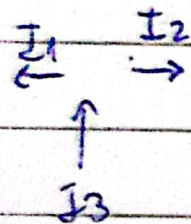


$$\textcircled{6} \quad \cancel{B} = \cancel{\mu_0} \cancel{H}$$

$$\phi_i = B(\pi r_i^2)$$

$$\frac{d\phi_i}{dt} = (\pi r_i^2) \frac{dB}{dt}$$



$$I_{6\Omega} = I_1 \quad I_{5\Omega} = I_3$$

$$I_{3\Omega} = I_2$$

$$\mathcal{E}_i = -\pi(r_i^2) \cdot 2$$

$$|\mathcal{E}_1| - 6I_1 - 3I_3 = 0$$

$$|\mathcal{E}_2| - 5I_2 - 3I_3 = 0$$

$$I_3 = I_1 + I_2$$


$$\begin{aligned} \mathcal{E}_1 &= -\pi \cdot (0,1)^2 \cdot 2 \\ &= -0,063 \text{ [V]} \end{aligned}$$

$$I_1 = 1,286 \text{ [mA]}$$

$$I_2 = 17,14 \text{ [mA]}$$

$$\begin{aligned} \mathcal{E}_2 &= -\pi (0,15)^2 \cdot 2 \\ &= -0,141 \text{ [V]} \end{aligned}$$

$$I_3 = 18,43 \text{ [mA]}$$

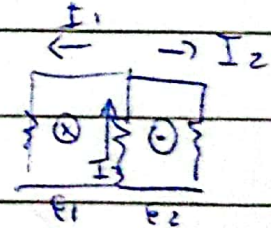

$$\mathcal{E}_1 - R_1 I_1 - R_3 I_3 = 0$$

$$\mathcal{E}_2 - R_2 I_2 - R_3 I_3 = 0$$